

Problem 8.1

$$\begin{aligned} \text{a) } I_{REF} = I_{D1} = I_{D2} &\Rightarrow I_{REF} = \frac{k_n}{2} (V_1 - V_2 - V_{TN})^2 [1 + \lambda_n (V_1 - V_2)] \\ &= \frac{k_n}{2} (V_2 - V_{TN})^2 (1 + \lambda_n V_2) \end{aligned}$$


$$\Rightarrow V_1 = 2V_2, \quad V_2 = 1.4351V, \quad V_1 = 2.8703V$$

$$\begin{aligned} \text{b) } I_{D3} = I_{D4} &\Rightarrow \frac{k_n}{2} (V_1 - V_3 - V_{TN})^2 (1 + \lambda_n (V_{out} - V_3)) \\ &= \frac{k_n}{2} (V_2 - V_{TN})^2 (1 + \lambda_n V_3) \end{aligned}$$

$$\Rightarrow V_{out} = \frac{1}{\lambda_n} \left[\frac{(V_2 - V_{TN})^2 (1 + \lambda_n V_3)}{(V_1 - V_3 - V_{TN})^2} - 1 \right] + V_3$$

$$\text{c) } M_3: V_1 - V_{TN} < V_{out} \quad M_4: V_2 - V_{TN} < V_3$$

$$\Rightarrow V_{out} > 2.3703V$$

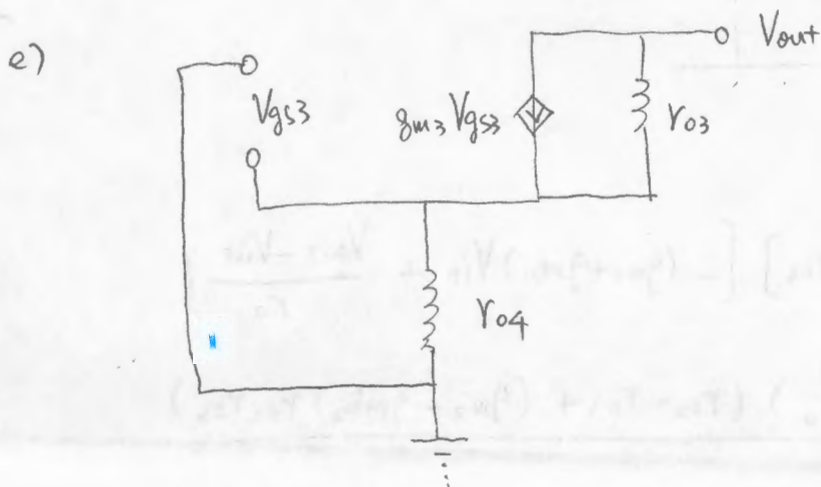


$$\text{f) } r_{oc} = r_{03} + r_{04} + g_{m3} r_{03} r_{04}$$


$$\text{g) } g_0 = \lambda_n I_D \Rightarrow r_{03} = r_{04} = 10000\Omega$$

$$g_{m3} = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})} = 0.0021S$$


$$r_{oc} = 2.3387 \times 10^5 \Omega$$

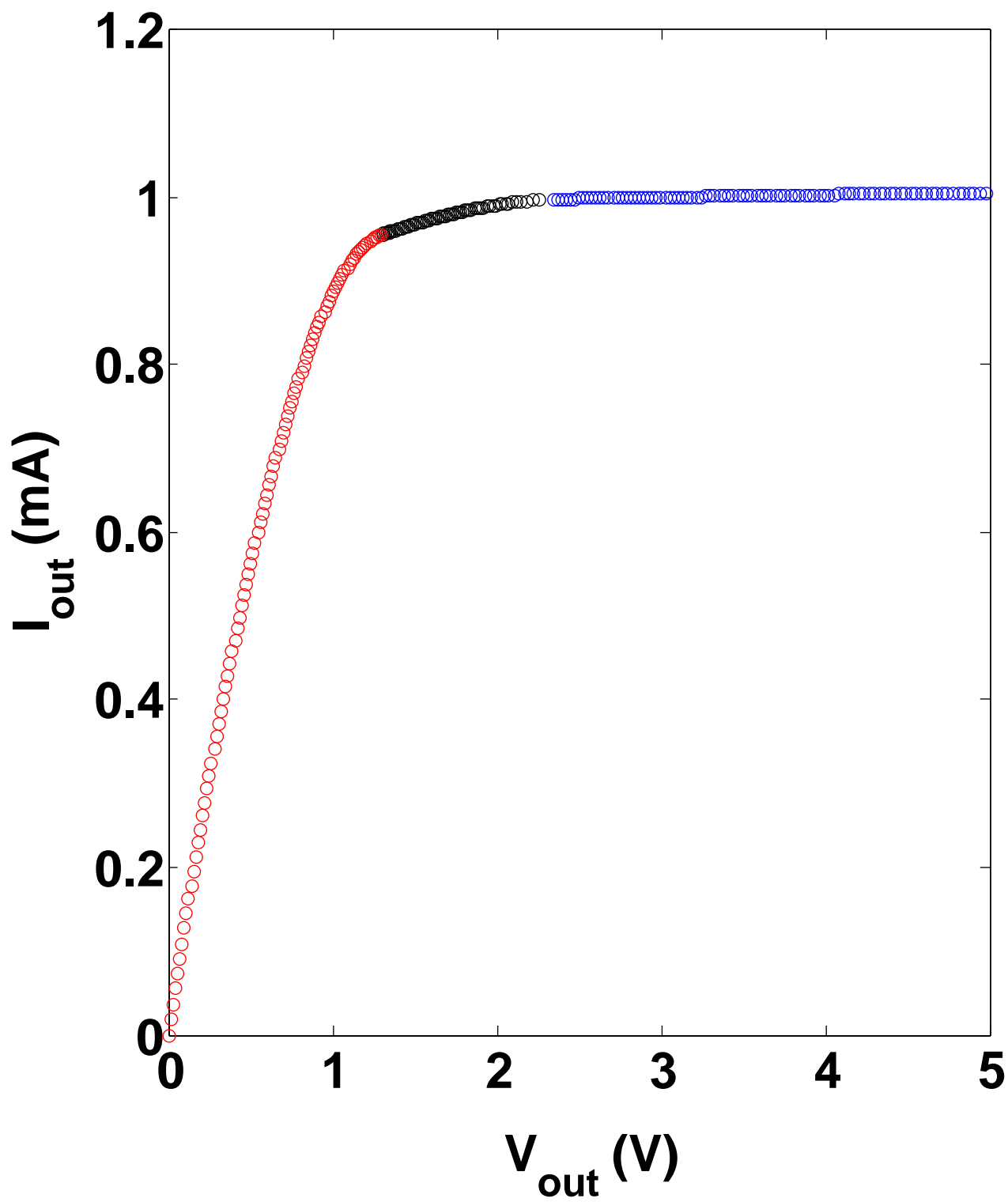

Problem 8.2

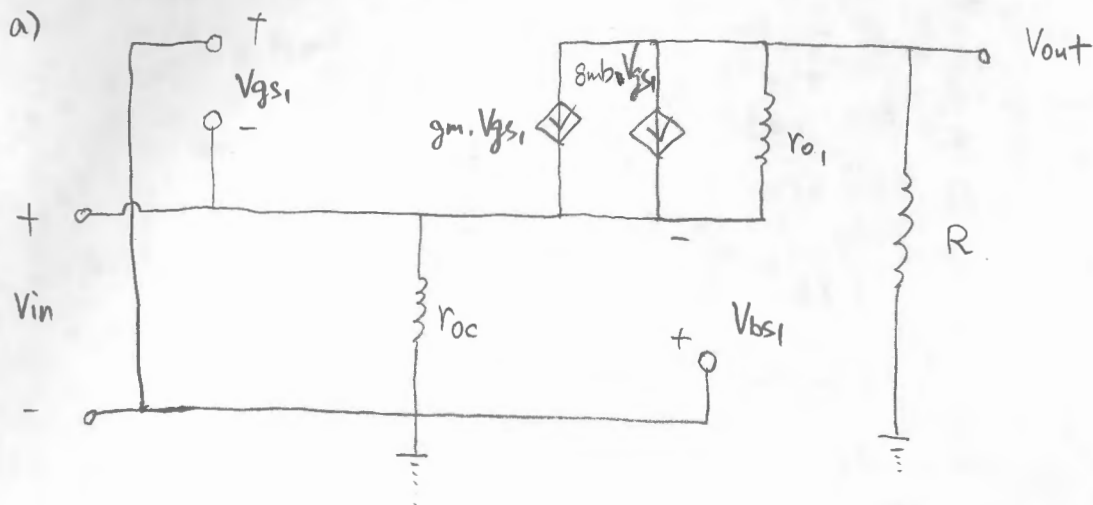

The circuit for R :

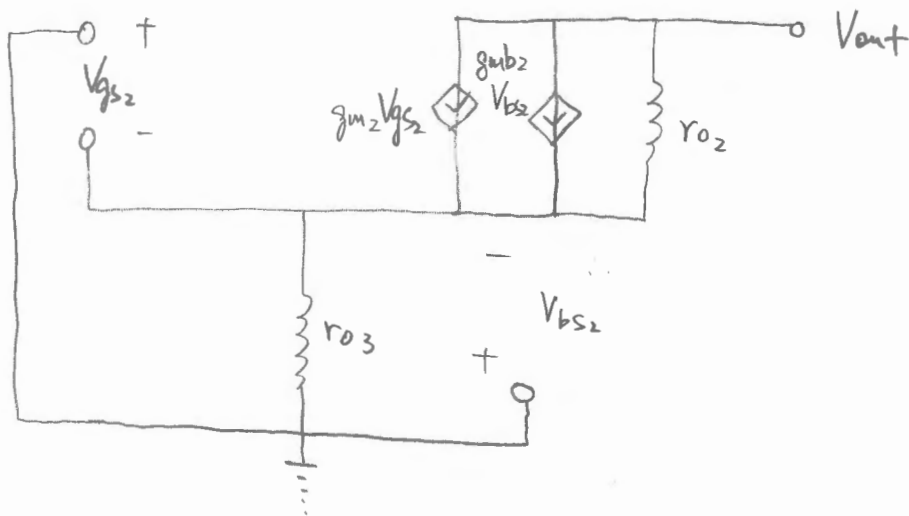


$$R = r_{o2} + r_{o3} + (g_{m2} + g_{mb2}) r_{o2} r_{o3}$$

$$V_{out} = -i_d R = -R \left[-(g_{m1} + g_{mb1}) V_{in} + \frac{V_{out} - V_{in}}{r_{o1}} \right]$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{(g_{m1} + g_{mb1} + \frac{1}{r_{o1}}) R}{1 + \frac{R}{r_{o1}}}$$

b)

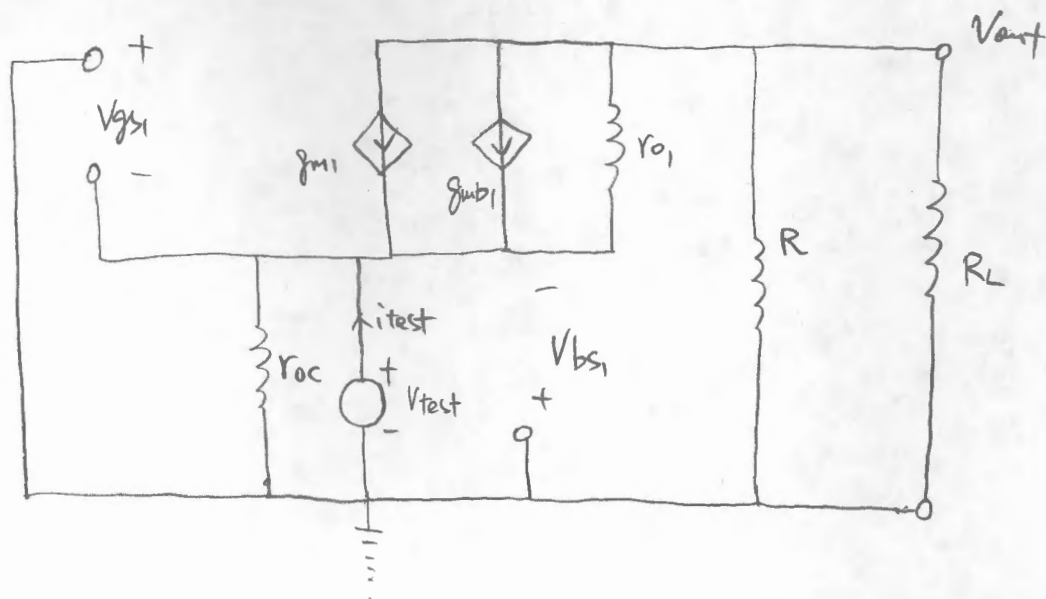


$$i_{test} = (g_{m1} + g_{mb1}) V_{test} - \frac{V_{out} - V_{test}}{r_{o1}} + \frac{V_{test}}{r_{oc}}$$

$$= (g_{m1} + g_{mb1} + \frac{1}{r_{oc}}) V_{test} - \frac{1}{r_{o1}} \left[\frac{(g_{m1} + g_{mb1} + \frac{1}{r_{o1}}) (R // R_L)}{1 + \frac{R // R_L}{r_{o1}}} - 1 \right] V_{test}$$

$$\Rightarrow R_{in} = \frac{V_{test}}{i_{test}} = \frac{(g_{m1} + g_{mb1}) r_{o1} + \frac{r_{o1} + R // R_L}{r_{oc}} + 1}{r_{o1} + R // R_L}$$


c)

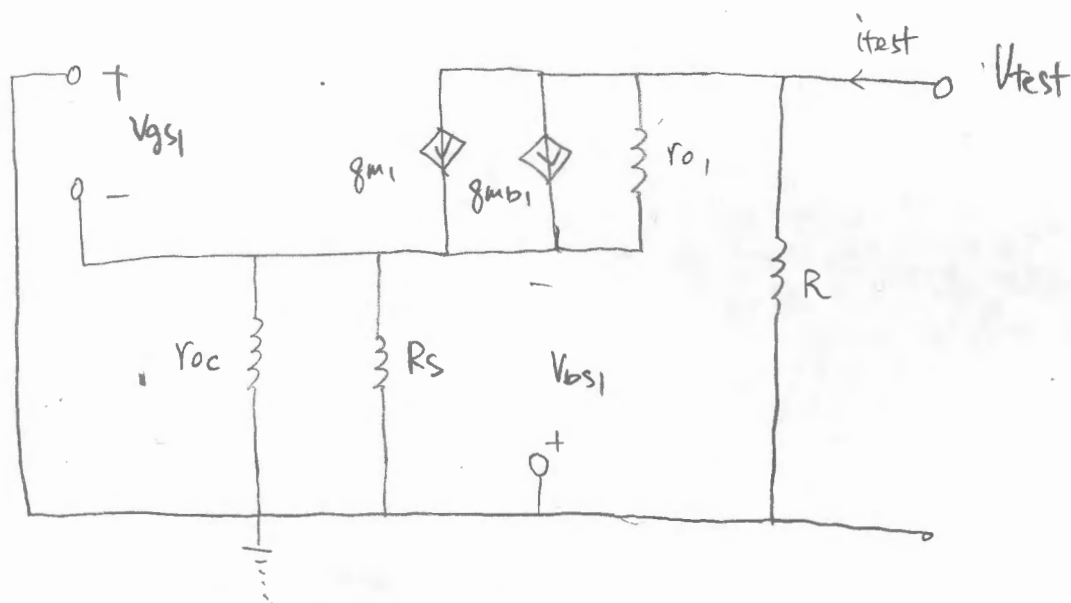

$$i_{test} = i_d + \frac{V_{test}}{R} = \frac{V_{test}}{R} + \frac{V_{test}}{r_{o1}} \left/ \left[1 + \frac{r_{oc} // R_s}{r_{o1}} + (g_{m1} + g_{mb1}) (r_{oc} // R_s) \right] \right.$$

$$\Rightarrow R_{out} = \frac{V_{test}}{i_{test}} = \frac{1}{R} + 1 / \left[r_{o1} + r_{oc} // R_s + (g_{m1} + g_{mb1}) r_{o1} (r_{oc} // R_s) \right]$$

Problem 8.4

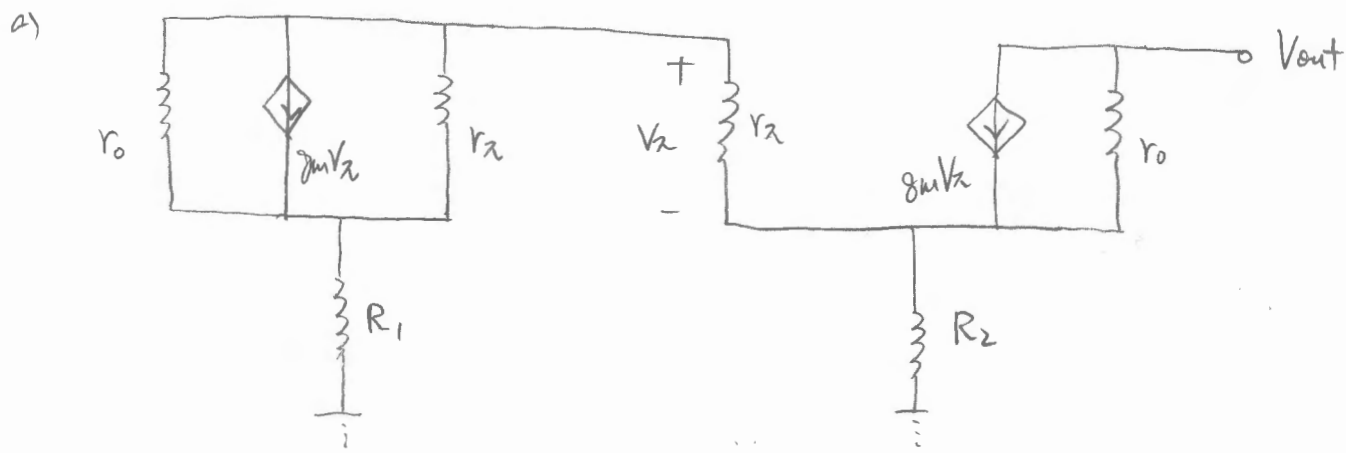

According to the lecture notes,

$$r_{oc} = \frac{V_{test}}{i_{test}} = \frac{\frac{r_o}{R_2} + \frac{(1+g_m r_x) r_o}{R+r_x} + 1}{\frac{1}{R_2} + \frac{1}{R+r_x}}$$

where $R = \left[(r_o \parallel \frac{1}{g_m} \parallel \frac{1}{r_x}) + R_1 \right]$


b) $V_{CE} > V_{CE-SAT} \Rightarrow V_{out} - (1 + \frac{1}{\beta_F}) I_{out} R_2 > V_{CE-SAT} + V_{BE-ON}$

$$\Rightarrow V_{out} > V_{CE-SAT} + V_{BE-ON} + (1 + \frac{1}{\beta_F}) I_{out} R_2$$


8.3

a) The Small Signal model becomes (assuming the output resistance of the current source is ∞)


$$r_{oc} = \frac{V_t}{i_t}$$

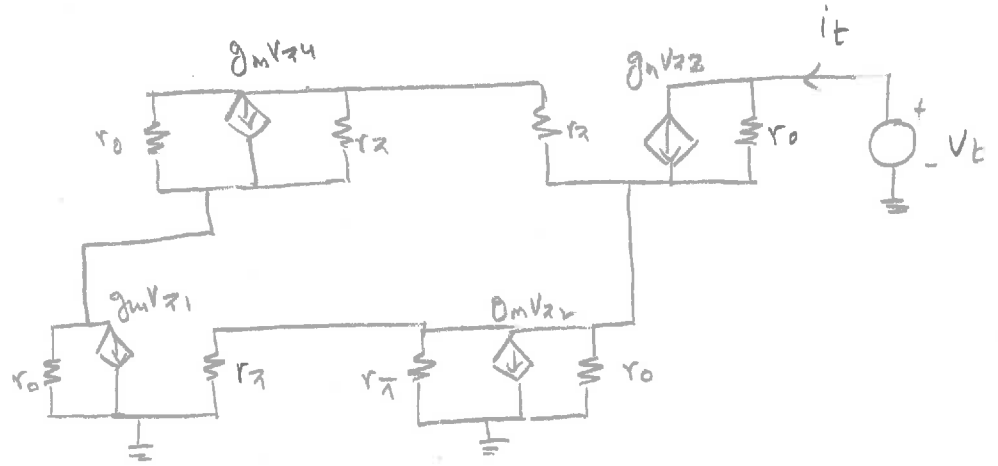

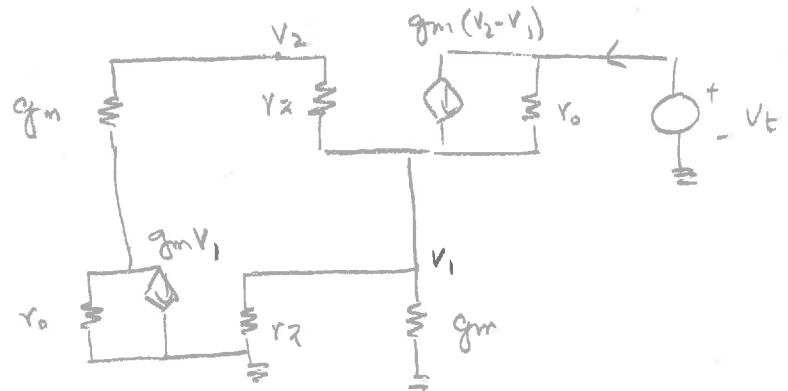The BJTs B_1 and B_2 are diode connected and their circuits can be replaced by conductances g_m to get.



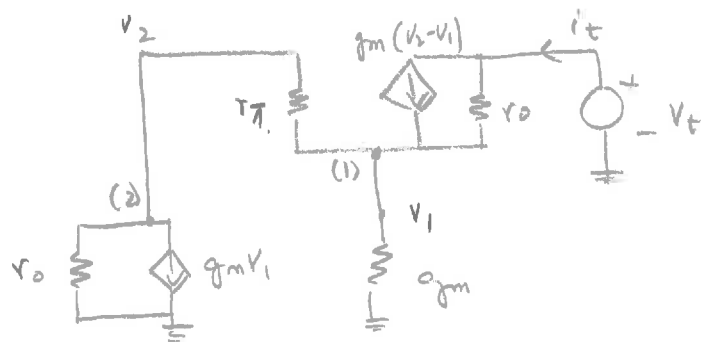This can be further simplified (since $g_m \gg g_{\pi} = \frac{1}{r_{\pi}}$):



KCL at (1) gives:

$$i_t = \frac{v_t - v_1}{r_o} + g_m (v_2 - v_1) = g_m v_1 + \frac{v_1 - v_2}{r_{\pi}} \Rightarrow \frac{v_t - v_1}{r_o} + g_m (v_2 - v_1) \approx g_m v_1$$

KCL at (2) gives:

$$\frac{v_1 - v_2}{r_{\pi}} = g_m v_1 + \frac{v_2}{r_o}$$

$$\Rightarrow v_2 \approx -g_m (r_{\pi} \parallel r_o) v_1$$

$$\Rightarrow v_2 - v_1 \approx -[g_m (r_{\pi} \parallel r_o) + 1] v_1$$

\Rightarrow

$$\frac{v_t}{r_o} = \frac{v_1}{r_o} - g_m (v_2 - v_1) + g_m v_1$$

$$\Rightarrow v_t \approx v_1 [1 + g_m r_o + g_m r_o [g_m (r_{\pi} \parallel r_o) + 1]]$$

$$i_t = g_m v_1 + \frac{v_1 - v_2}{r_{\pi}} \approx \left[g_m + \frac{g_m (r_{\pi} \parallel r_o) + 1}{r_{\pi}} \right] v_1$$

$$\Rightarrow i_t \approx g_m \left[1 + \frac{(r_{\pi} \parallel r_o)}{r_{\pi}} \right] v_1 = g_m \left[1 + \frac{(r_{\pi} \parallel r_o)}{r_{\pi}} \right] \frac{v_t}{\left[1 + 2g_m r_o + g_m r_o [g_m (r_{\pi} \parallel r_o)] \right]}$$

$$\Rightarrow r_{oc} \approx \frac{\left[1 + 2g_m r_o + g_m r_o [g_m (r_{\pi} \parallel r_o)] \right]}{g_m \left[1 + \frac{(r_{\pi} \parallel r_o)}{r_{\pi}} \right]} \approx \frac{g_m (r_{\pi} \parallel r_o)}{\left[1 + \frac{(r_{\pi} \parallel r_o)}{r_{\pi}} \right]} r_o \approx \frac{\beta_F r_o}{2} \quad \downarrow$$

(if $r_o \gg r_{\pi}$)

b) $V_{OUT} > V_{BE-ON} + V_{CE-SAT}$