

Problem 10.1

a) CE & CB.

b) B3 is the biasing current source.

B4 is a current mirror, providing the biasing voltage of B3.

c) B5 is to provide the proper voltage bias for B2.

d) Common emitter amplifier, with emitter degeneration. It provides a large input resistance for the amplifier.

e) Common base amplifier, providing a large voltage gain.


$$f) V_2 = V_{DD} - V_{BE_ON} = 5.0V - 0.7V = 4.3V$$

$$V_3 = V_{DD} - 2V_{BE_ON} = 5.0V - 1.4V = 3.6V$$

$$V_1 = V_3 + V_{BE_ON} = 3.6V + 0.7V = 4.3V$$

$$g) V_{BIAS} = \frac{I_{BIAS}}{2} R_E + V_{BE_ON} = 0.1V + 0.7V = 0.8V$$

h) & i)

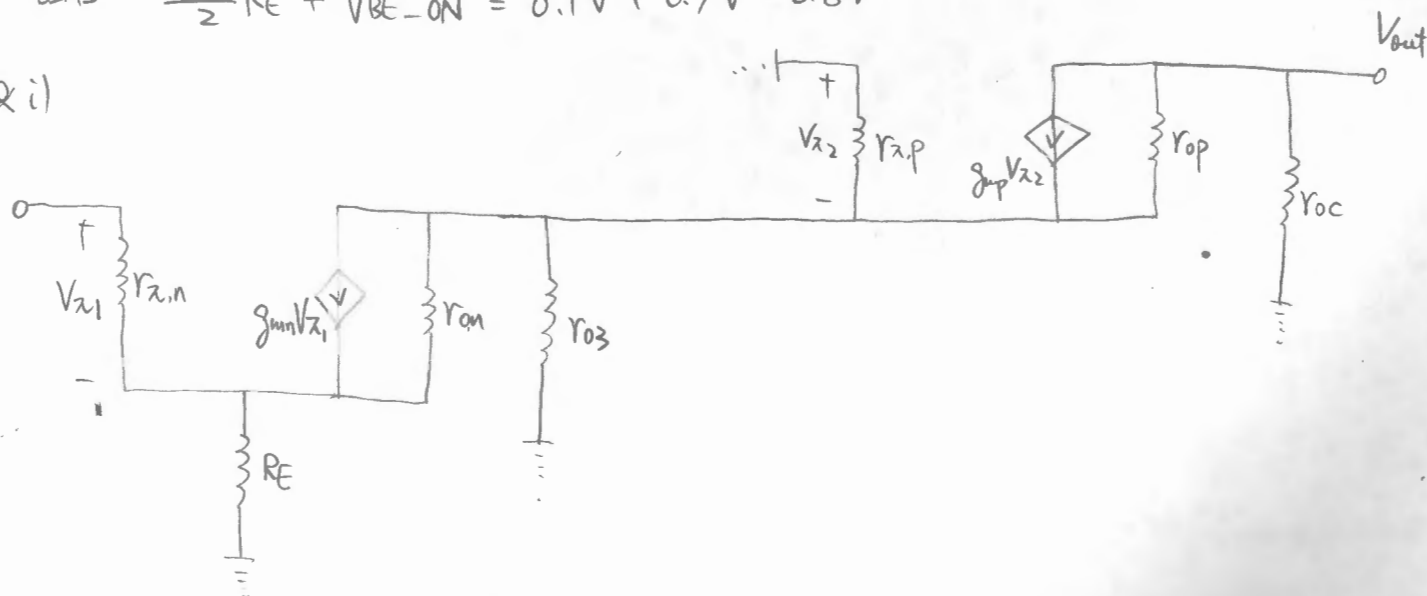

The small signal model is a cascade of two stages.

First stage

$$A_{v1} = \frac{V_{out}}{V_{in}} = -g_m \frac{r_{o,n} \parallel r_{o3}}{1 + g_m R_E \frac{r_{o,n}}{r_{o,n} + r_{o3}}}$$

$$R_{out1} = (r_{o,n} \parallel r_{o3}) \frac{1 + g_m R_E}{1 + g_m R_E \frac{r_{o,n}}{r_{o,n} + r_{o3}}}$$

Second stage

$$A_{v2} = g_{mp} (r_{op} \parallel r_{oc}) = \frac{V_{out}}{V_{in}} \quad R_{in2} = \frac{1}{g_{mp}} \left(1 + \frac{r_{oc}}{r_o} \right)$$

For the whole circuit

$$V_{out} = A_{v2} \frac{R_{in2}}{R_{in2} + R_{out1}} V_{in} A_{v1} \Rightarrow A_v = A_{v1} A_{v2} \frac{R_{in2}}{R_{in2} + R_{out1}}$$

The output resistance of the circuit is the output resistance of CB with R_{out1} .

$$\frac{1}{R_{out}} = \frac{1}{r_{oc}} + \frac{r_{op} \parallel \frac{r_{zp}}{1 + \beta_F} \parallel R_{out1}}{r_{op} (r_{zp} \parallel R_{out1})}$$



Problem 10.2

a) CC & CB

$$b) V_{BIAS1} \geq V_{out} + V_{CE-SAT} + V_{BE-ON} = 3.0V + 0.2V + 0.7V = 3.9V$$

$$V_{BIAS2} = V_{BIAS1} - V_{BE-ON} - V_{BE-ON} \geq 3.9V - 1.4V = 2.5V$$

c) & d) Two stages.

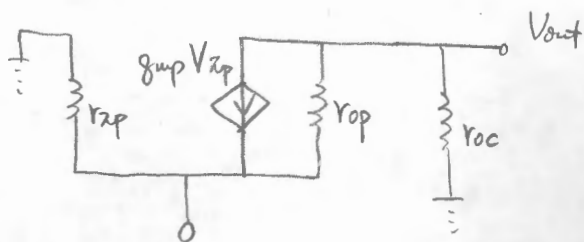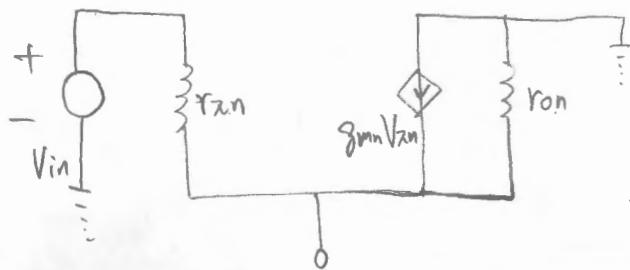

Second stage:

$$A_{v2} = g_{mp} (r_{op} \parallel r_{oc}) \quad R_{in2} = \frac{1}{g_{mp}} \left(1 + \frac{r_{oc}}{r_o} \right)$$

First stage:

$$A_{v1} = 1 \quad R_{out1} = \frac{1}{g_{mn}}$$

For the whole circuit.


$$A_v = \frac{V_{out}}{V_{in}} = A_{v1} A_{v2} \frac{R_{in2}}{R_{in2} + R_{out1}}$$

$$\text{The output resistance} \quad \frac{1}{R_{out}} = \frac{1}{r_{oc}} + \frac{r_{op} \parallel \frac{r_{xp}}{1 + \beta_F} \parallel R_{out1}}{r_{op} (r_{xp} \parallel R_{out1})}$$


10.3

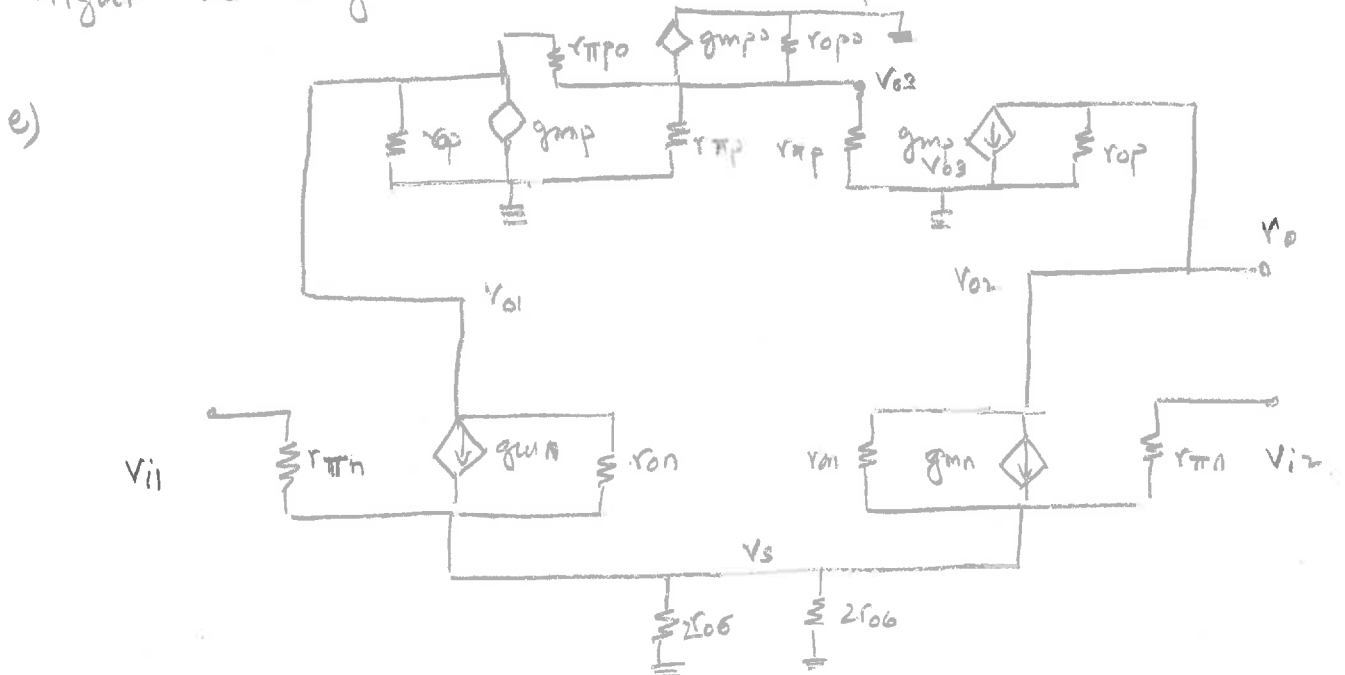a) M7 provides for the bias currents of M3 and M4 and ensures that the drain currents of M1 and M2 are matched accurately.

Might be a good idea to solve parts (e) and (f) next.



First look at this part:

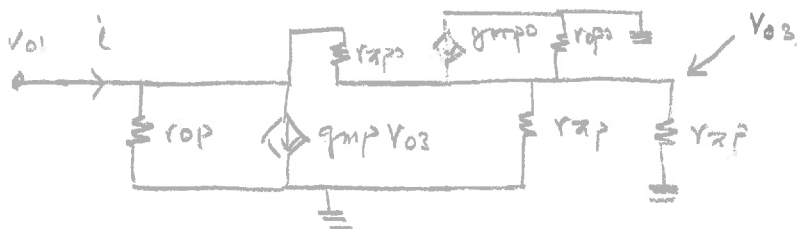

- M3, M7 and M4
- r_{o7} , g_{m7} and r_{o7} belong to M7.

What is V_{o3} in terms of V_{o1} ?

What is the current i ?

Note that $|I_{C7}| \approx |I_{E7}| = 2I_{B3} = 2I_{B4}$

$$\Rightarrow g_{m7} = \frac{qI_{C7}}{kT} = 2g_{m3}$$

We have (KCL at node V_{o3}):

$$(V_{o1} - V_{o3})g_{\pi p0} + g_{m p0}(V_{o1} - V_{o3}) + (0 - V_{o3})g_{o p0} = V_{o3} 2g_{\pi p}$$


$$\Rightarrow V_{o3} \approx V_{o1} \frac{g_{m p0}}{g_{m p0} + 2g_{\pi p}} = \frac{V_{o1}}{2}$$

$$\text{Also: } i = V_{o1} g_{o p} + g_{m p} V_{o3} + (V_{o1} - V_{o3}) g_{\pi p0}$$

$$\approx V_{o1} g_{o p} + g_{m p} \frac{V_{o1}}{2} + \frac{V_{o1}}{2} g_{\pi p0}$$

$$\approx \frac{g_{m p}}{2} V_{o1}$$

So we can redraw the circuit:

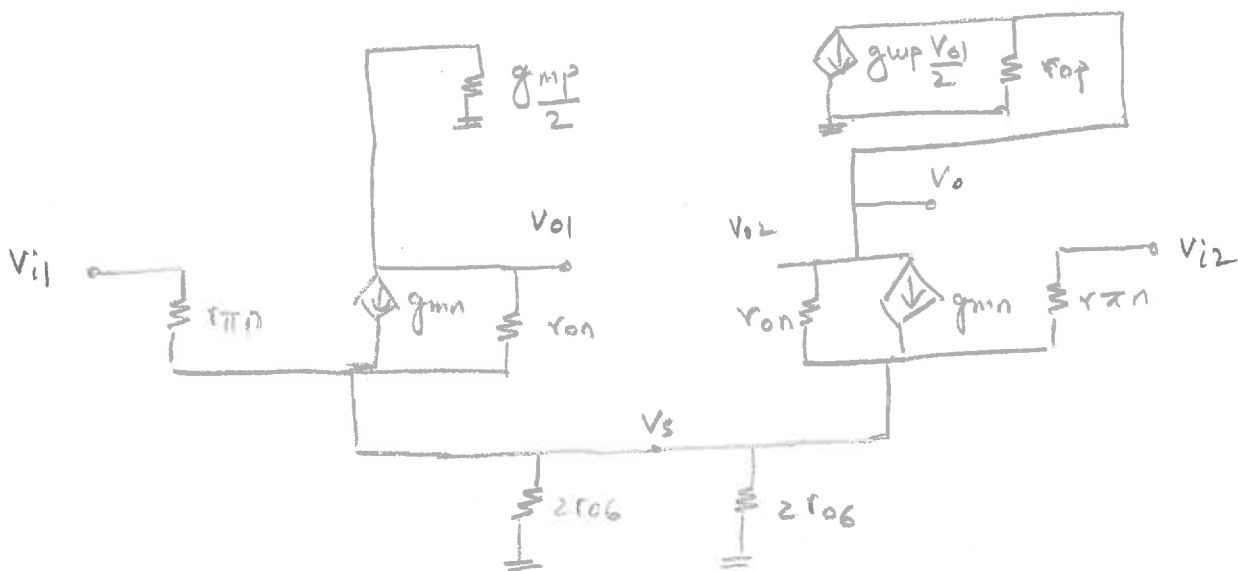

$$\text{Now suppose } V_{i1} = \frac{V_{id}}{2} \quad V_{i2} = -\frac{V_{id}}{2}$$

KCL at node V_{o1} gives:

$$V_{o1} \frac{g_{m p}}{2} + g_{m n} \left(\frac{V_{id}}{2} - V_s \right) + \underbrace{(V_{o1} - V_s) g_{o n}}_{\text{small compared to } V_{o1} \frac{g_{m p}}{2}} = 0$$

KCL at node V_{o2} gives:

$$V_{o2} g_{op} + g_{mp} \frac{V_{o1}}{2} + (V_{o2} - V_s) g_{on} + g_{mn} \left(-\frac{V_{id}}{2} - V_s \right) = 0$$

Subtract the above eq. from the previous one:

$$g_{mn} V_{id} - V_{o2} (g_{op} + g_{on}) = 0$$

$$\Rightarrow V_{o1} - V_{o2} = g_{mn} (r_{op} || r_{on}) V_{id}$$

$$\Rightarrow A_{vd} = \frac{V_o}{V_{id}} = g_{mn} (r_{op} || r_{on})$$

f) Now suppose $V_{i1} = V_{i2} = V_{ic}$

The current mirror will ensure that the collector currents of M_1 and M_2 are the same when $V_{i1} = V_{i2} = V_{ic}$.

Therefore, we can safely assume that the two halves are perfectly symmetric and that no current flows in the bottom wire connecting the two halves. The left half is now a CE amplifier with a degenerate emitter, and we set (approximations made in the handouts assume R_E is small and will not work here):

$$\frac{V_{o1}}{V_{ic}} \approx - \frac{\frac{2g_{mn}}{g_{mp}}}{1 + \frac{2r_{o6}}{(r_{\pi n} \parallel r_{o1})} + g_{mn}(2r_{o6})}$$

Since the circuit is symmetric, $V_{o1} \approx V_{o2}$

$$\Rightarrow \frac{V_o}{V_{ic}} = \frac{V_{o1}}{V_{ic}} \approx - \frac{\frac{2g_{mn}}{g_{mp}}}{1 + \frac{2r_{o6}}{(r_{\pi n} \parallel r_{o1})} + g_{mn}(2r_{o6})}$$

b) When $V_{i1} = \frac{V_{id}}{2} = -V_{i2}$, $V_s \approx 0$ and $R_{in} \approx r_{\pi n}$.

c) When $V_{i1} = V_{ic} = V_{i2}$, each half is a CE amplifier with a degenerate emitter. So R_{in} becomes (analysis in the handouts assume R_E is small and will not work here).

$$R_{in} = r_{\pi n} + 2r_{o6} + \frac{2r_{o6} g_{mn} r_{o1} r_{\pi n}}{r_{o1} + 2r_{o6}}$$

$$\approx r_{\pi n} \left[1 + \frac{g_{mn} r_{o1} (2r_{o6})}{r_{o1} + 2r_{o6}} \right] + 2r_{o6}$$

d) Suppose $V_{i1} = \frac{V_{id}}{2} = -V_{i2}$. First we find the short circuit output current.

KCL at node V_{o1} gives:

$$V_{o1} \frac{g_{mp}}{2} + g_{mn} \left(\frac{V_{id}}{2} - V_s \right) + \underset{\substack{\uparrow \\ \text{small}}}{(V_{o1} - V_s) g_m} = 0$$

KCL at node V_{o2} gives (include i_{out}):

$$V_{o2} g_{op} + g_{mp} \frac{V_{o1}}{2} + (V_{o2} - V_s) g_{on} + g_{mn} \left(-\frac{V_{id}}{2} - V_s \right) + i_{out} = 0$$

But output is shorted to ground, so $V_o = V_{o2} = 0$.

$$g_{mp} \frac{V_{o1}}{2} - V_s g_{on} + g_{mp} \left(-\frac{V_{id}}{2} - V_s \right) + i_{out} = 0.$$

Subtract from the above equation obtained for node V_{o1} :

$$g_{mp} V_{id} - i_{out} = 0$$

$$\Rightarrow i_{out} = g_{mp} V_{id}$$

Now we use: $\left\{ \text{short circuit output current} \right\} R_{out} = \left\{ \text{open circuit output voltage} \right\}$

$$\Rightarrow g_{mn} V_{id} R_{out} = g_{mn} (r_{op} \parallel r_{on}) V_{id}$$

$$\Rightarrow R_{out} = (r_{op} \parallel r_{on})$$