


# ECE 3150 Lab 2

Aalaap Narasipura


February 26, 2016

## 1 Pre-Lab Work

### CMOS Logic Inverter

 

 
- a)  $V_{OUT} < V_{IN} - V_{TN}$
- b)  $V_{OUT} > V_{IN} - V_{TN}$
- c)  $V_{IN} < V_{TN}$
- d)  $V_{OUT} > V_{IN} - V_{TP}$
- e)  $V_{OUT} < V_{IN} - V_{TP}$
- f)  $V_{IN} > V_{TP} + V_{DD}$
- g)  $V_{DD} = 5.0V$ ,  $V_{TN} = 1.5V$ ,  $V_{TP} = -1.5V$ , finally,  $k_n = k_p$




1. NFET in cutoff region, PFET is in linear region
2. NFET in saturation region, PFET is in linear region
3. Both are in saturation
4. NFET in linear region, PFET is in saturation region
5. NFET in cutoff linear, PFET is in cutoff region

## 2 Post Lab Work

### 2.1 Transconductance

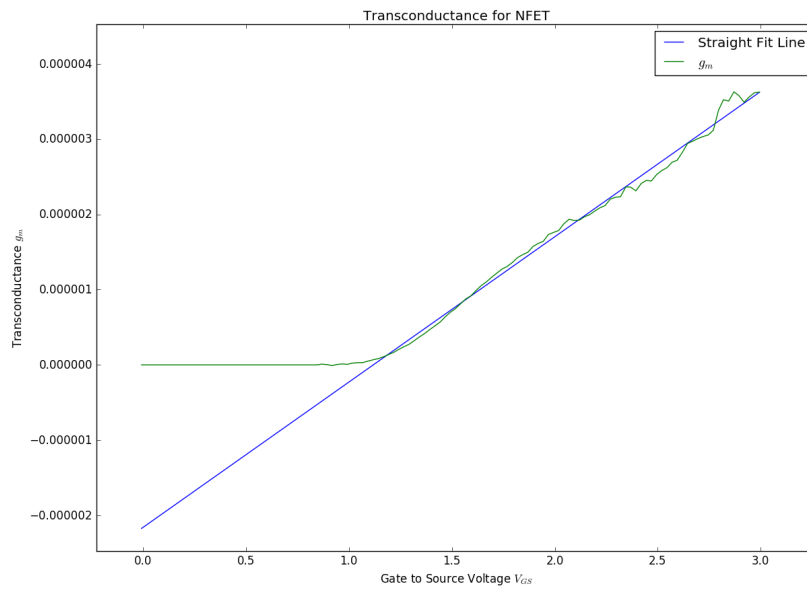

 Equation of line fit =  $y = 1.93177 * 10^{-6}x - 2.1607 * 10^{-6}$



Equation of line fit =  $y = -.0006996x - .0009546$


$$V_{tn} = 1.118V, k_n = 1.93177 * 10^{-6} \frac{A}{V^2}$$

$$V_{tp} = -1.42V, k_p = -.0006996 \frac{A}{V^2}$$

The NFET and PFET were not in agreement. I am not entirely sure why the NFET data is so much different. I think that we may have damaged the NFET at some point by having too large of a bias voltage or messing up the sweep voltage. However with this being said.


The shape of the curve is what we want.  $k_p$  is the correct value based on the transistor data sheet given to us.

## 2.2 Subthreshold Condition

 

The measured inverse slope value was  $175 \frac{mv}{dec}$


## 2.3 FET Output Curves

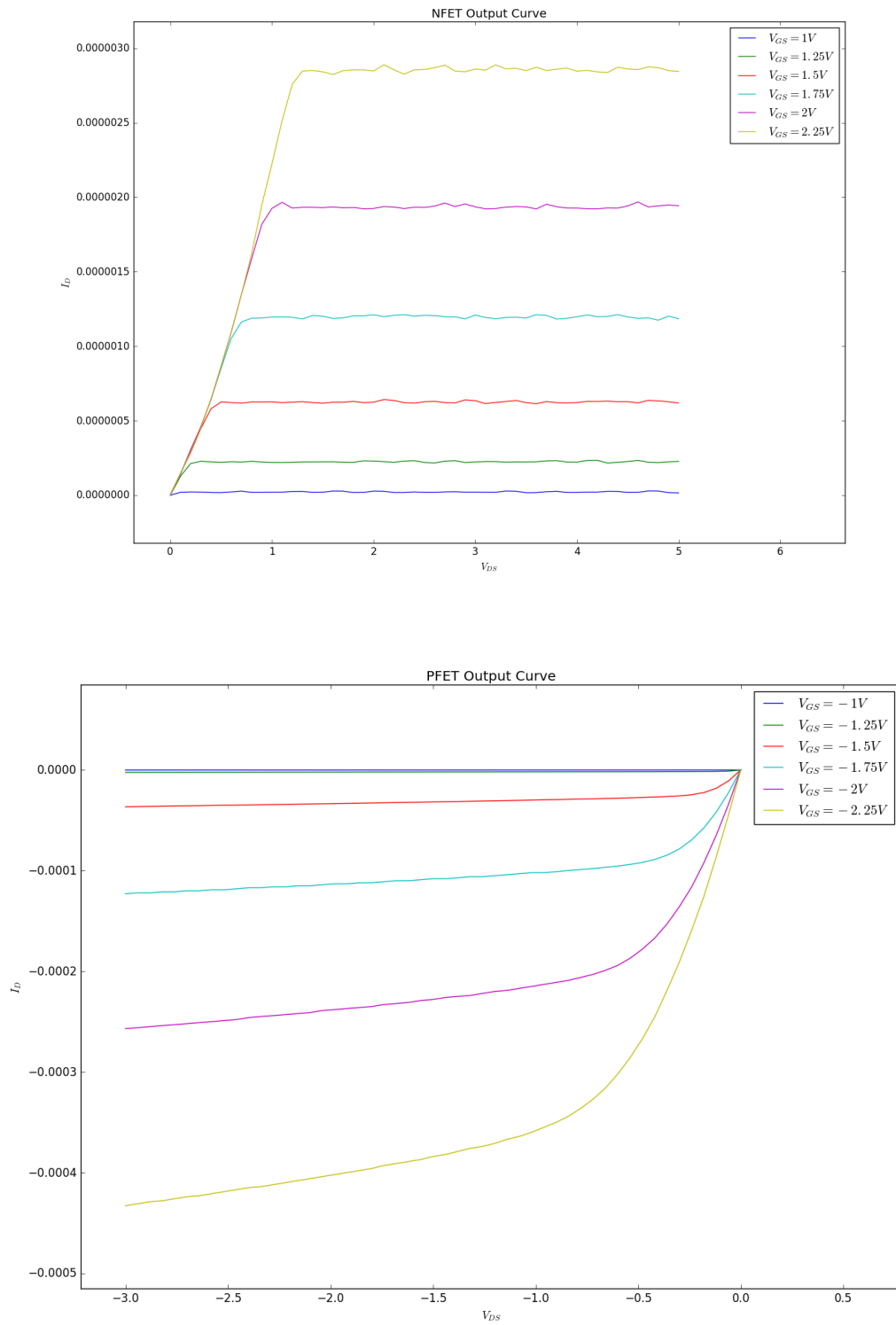


The slope of the PFET output curve above threshold was larger due to a larger channel

length modulation. The NFET seemingly has a much smaller output current compared to the PFET, but this I believe is due to a damaged NFET. However if you were to scale the NFET data up so it was the same order of magnitude as the PFET it would have larger magnitude output current for a given  $V_{GS}$ .

## 2.4 FET Output Conductance

 

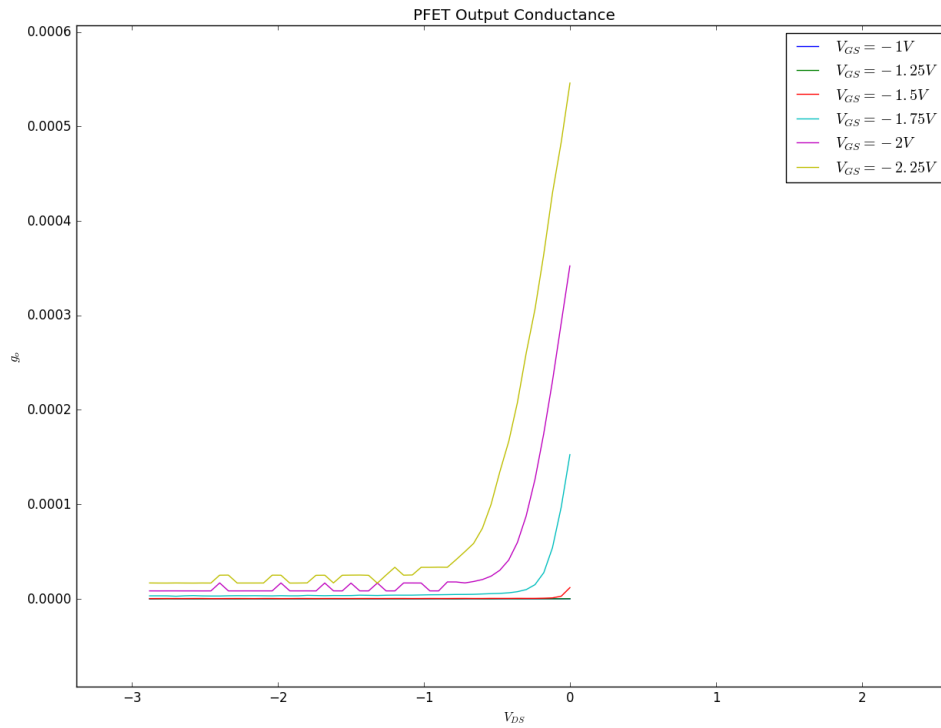
Again the values of  $g_o$  we got were quite off when compared to the PFET. We know the PFET is correct because I compared the values we got to the transistor data sheet. There is also a lot more noise in the NFET data. Both may be due to a damaged NFET. Also I noticed an odd taper down for the NFET.



The PFET data shows only up to -3V. However because there will not be much output conductance at voltages less than  $V_{TP}$ , it can be extrapolated that from -3 V to -5V the data will be very similar if not exact to the values from -2V to -3 V.

I graphed more plots than the post lab said to do because I found it very interesting that at -1V  $V_{GS}$  and -1.25V  $V_{GS}$  for the PFET that there was almost no output conductance. A similar thing happened with the NFET for 1V  $V_{GS}$


## 2.5 Diode-Connected NFET

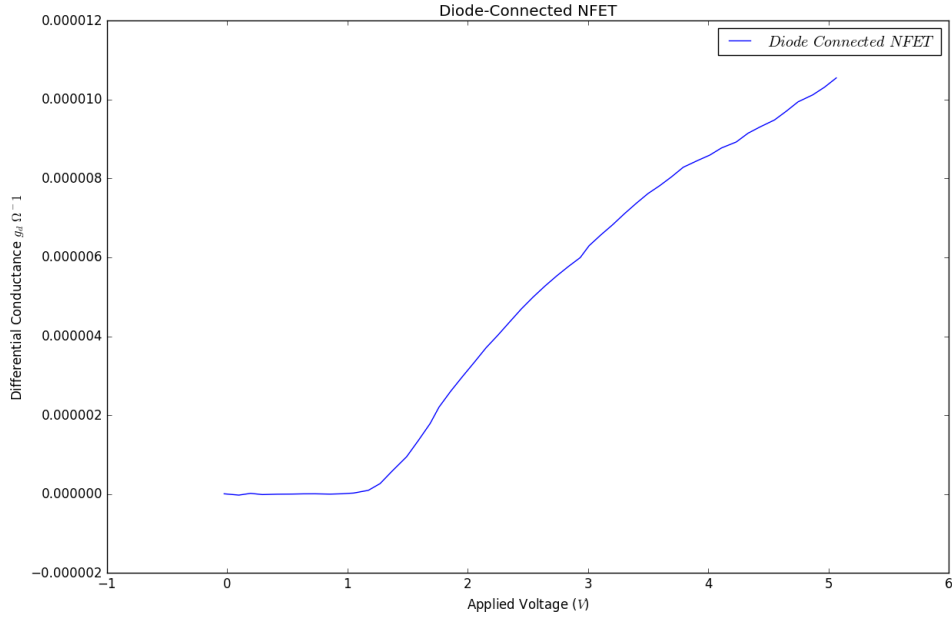

The differential conductance that we measured follows the same path as the plot of transconductance in 2.1. The differential conductance bows out away from transconductance plot/ data. However the data values of the Diode-Connected This shows that is only an approximation of the transconductance we measured. It makes sense that these plots are similar because it is still an NFET device.



## 2.6 CMOS Inverter

 

1. NFET in cutoff region, PFET is in linear region
2. NFET in saturation region, PFET is in linear region
3. Both are in saturation
4. NFET in linear region, PFET is in saturation region
5. NFET in cutoff linear, PFET is in cutoff region

Due to the damaged NFET that we have the the CMOS inverter diagram is also incorrect. It again follows the correct shape but the  $V_{TN}$  value is very much off.