

Problem 9.1

- a) The transconductance of the cascode amplifier is approximately the transconductance of M_1 . To make

$$g_{m1} = \sqrt{2k_n I_D} \approx 1 \text{ mS} \Rightarrow W_1 = 200 \mu\text{m}$$

b) $M_1: R_{out} \approx r_{o1} = (\lambda_n I_D)^{-1} = 200 \text{ k}\Omega$

$M_2: R_{out} \approx g_{m2} r_{o1} r_{o2}$

$M_3: R_{out} \approx g_{m3} r_{o3} r_{o8}$

$M_8: R_{out} \approx r_{o8} = (\lambda_p I_D)^{-1} = 500 \text{ k}\Omega$

c) $R_{out} \approx g_{m2} r_{o1} r_{o2} = 20 \text{ M}\Omega \Rightarrow g_{m2} = 0.5 \text{ mS}$

d) $g_{m2} = \sqrt{2k_n I_D} = 0.5 \text{ mS} \Rightarrow W_2 = 50 \mu\text{m}$

e) $R_{out} = g_{m3} r_{o3} r_{o8} = 100 \text{ M}\Omega \Rightarrow g_{m3} = 0.4 \text{ mS}$

f) $g_{m3} = \sqrt{2k_p I_D} = 0.4 \text{ mS} \Rightarrow W_3 = 64 \mu\text{m}$

g) $W_4 = W_3 = 64 \mu\text{m}, W_5 = W_2 = 50 \mu\text{m}, W_6 = W_8 = W_3 = 64 \mu\text{m}$

i) $V_1: -I_{D1} = -\frac{W_1}{2L} \mu_p C_{ox} (V_1 - V_{DD} - V_{TP})^2 \Rightarrow V_1 = 3.5 \text{ V}$

$V_2: -I_{D1} = -\frac{W_4}{2L} \mu_p C_{ox} (V_2 - V_1 - V_{TP})^2 \Rightarrow V_2 = 2 \text{ V}$

$V_3 = V_2 = 2 \text{ V}$

j) $V_4 = V_1 = 3.5 \text{ V},$

For V_6 :

$$I_{D1} = \frac{W_5}{2L} \mu_n C_{ox} (V_3 - V_6 - V_{TN})^2 \Rightarrow V_6 = 0.6V$$

For V_7 :

$$I_{D1} = \frac{W_6}{2L} \mu_n C_{ox} (V_7 - V_{TN})^2 \Rightarrow V_7 = 1.2V$$

h) $I_{D1} = \frac{W_7}{2L} \mu_n C_{ox} (V_7 - V_{TN})^2 \Rightarrow W_7 = W_6 = W_1 = 200 \mu m$

k) $V_{BIAS} = V_7 = 1.2V$

l) $R = \frac{V_{DD} - V_7}{I_{REF}} = 38000 \Omega$

Problem 9.2

a) CG, CS

b) $I_{BIAS1} = \frac{W_1}{2L} \mu_n C_{ox} (1.5 - V_2 - V_{TN})^2$, $V_2 = 0.5V \Rightarrow W_1 = 355 \mu m$

c) $-I_{BIAS3} = -\frac{W_2}{2L} \mu_p C_{ox} (V_1 - V_{DD} - V_{TP})^2$, $V_1 = 3.0V \Rightarrow W_2 = 160 \mu m$

d) The input resistance is the input resistance of CG amplifier with infinite load resistance.

$$R_{in} = \frac{1}{g_m} \left(1 + \frac{r_{oc1}}{r_o} \right) \text{ according to the lecture notes.}$$

e) The output resistance is the output resistance of CS amplifier,

$$R_{out} = r_{o2} \parallel r_{o3}$$


f)

$$R_m = \frac{V_{out}}{i_s} = R_{m1} \times A_{v2} = A_{i1} \times R_{out1} \times A_{v2} \approx r_{oc1} (-g_{m2} (r_{o2} \parallel r_{oc3}))$$

$$= -g_{m2} r_{oc1} (r_{o2} \parallel r_{oc3})$$

g)

Consider another CD cascade stage

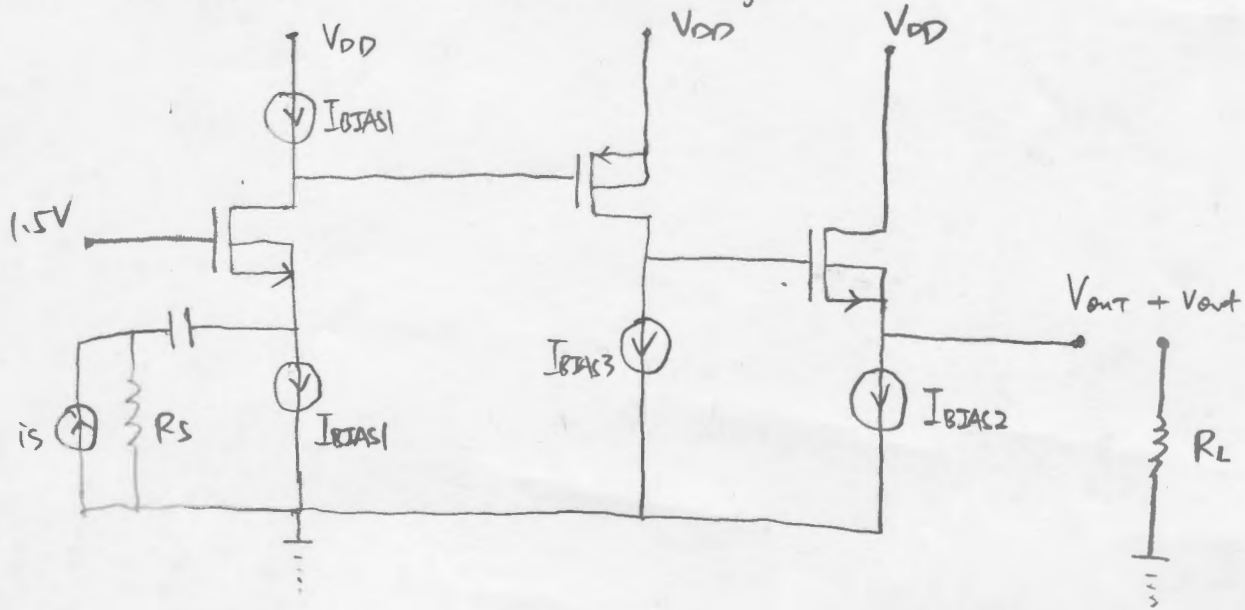

Because $V_{OUT} = 1.5V$, $V_{GS} = 2.5V - 1.5V = 1V$, NMOS is needed.

$$A_v = \frac{g_m R_o}{1 + g_m R_o}, \quad R_o = r_{oc2}$$

$$R_{out} = \frac{R_o}{1 + g_m R_o}, \quad V_{OUT} = R_o I_{BIAS2}$$

For $A_v \sim 1$, $R_{out} \sim 5k\Omega$, $g_m \sim 0.2mS$, $g_m = \sqrt{2k_n I_{BIAS2}}$.

If we have similar current sources, choose $I_{BIAS2} = 200\mu A$, then $W_n = 8\mu m$.

For $V_{OUT} = 1.5V$, $R_o \sim 7.5k\Omega$, on the order of R_s .

Problem 9.3

a) Considering the symmetry of the circuit and devices, the current through each leg is the same as $I_{REF} = 100 \mu A$

b) $Power = 5 \times 5V \times 100 \mu A = 2.5 mW$

c) $V_{BIAS} = V_5$

$$I_{REF} = \frac{W_n}{2L} \mu_n C_{ox} (V_5 - V_{TN})^2 \Rightarrow V_{BIAS} = V_5 = 1.5944V$$

d) $M_1 \& M_2$: CS & CB transconductance amplifier

M_3 : CD voltage buffer

M_4 : CC voltage buffer

e) For V_1 :

$$-I_{REF} = -\frac{W_p}{L} \mu_p C_{ox} (V_1 - V_{DD} - V_{TP})^2 \Rightarrow V_1 = 3.6675V$$

For V_2 :

$$-I_{REF} = -\frac{W_p}{L} \mu_p C_{ox} (V_2 - V_1 - V_{TP})^2 \Rightarrow V_2 = 2.3351V$$

For V_3 :

$$V_3 = V_2 - V_{BE_ON} = 2.3351 - 0.7V = 1.6351V$$

For V_4 :

$$V_4 = V_1 = 3.6675V$$

For V_5 :

$$V_5 = 1.5944V$$

For V_X :

$$V_X = V_2 = 2.3351V$$

For V_{out} :

$$V_{out} = V_4 - V_{BE_ON} = 3.6675V - 0.7V = 2.9675V$$

f) 8.8)
M10:

$$V_5 - V_{out} < V_{TN} \Rightarrow V_{out} > V_5 - V_{TN} = 0.8944V$$

Q4:

$$V_{CE} > V_{CE-SAT} \Rightarrow V_{DD} - V_{out} > V_{CE-SAT} \Rightarrow V_{out} < V_{DD} - V_{CE-SAT} = 4.8V$$

h) The circuit voltage gain is approximately the gain of the cascade of M_1 and Q_2 .

$$R_{out1} = r_{o1}, \quad R_{in2} = \frac{r_{\lambda 2}}{1 + (\beta_F r_{o2} / (r_{o2} + R))}, \quad \text{here } R = g_{m6} r_{o6} r_{o7} + r_{o6} + r_{o7}$$

$$A_{v1} = -g_{m1} r_{o1}, \quad A_{v2} = g_{m2} (R \parallel r_{o2}).$$

$$r_{o1} = (\lambda_n I_D)^{-1}, \quad I_D = I_{REF}, \quad g_{m1} = \sqrt{2k_n I_D}.$$

$$r_{\lambda 2} = \frac{K_T}{\beta_{IB}} = \frac{K_T}{\beta_{IC}} \beta_F, \quad I_C \approx I_{REF}, \quad \beta_F = \beta_{FO} e^{\frac{V_{CE}}{V_A}}, \quad V_{CE} = V_X - V_3$$

$$r_{o2} = \frac{V_A}{I_D}, \quad g_{m2} = \frac{\beta_{IC}}{K_T}$$

$$g_{m6} = g_{m1}, \quad r_{o6} = r_{o7} = r_{o1}$$

$$A_v = A_{v2} A_{v1} \frac{R_{in2}}{R_{out1} + R_{in2}} = -5.8 \times 10^3$$